

SYNTAX

~~tran~~ .tran

sampling gap
<T0>

display range
<R0>

UIC
classical initial condition

Date

Page

CODE:- (Transient analysis)

Series RL circuit <first line does not interpret>

V 1 0 DC 1

R 1 2 2K

L 2 0 50m

.tran 2.5u 250u UIC

.probe

.end ~~Time constant~~




$\frac{L}{R}$

$R \times C$


4/8/23

LAB DAY 2

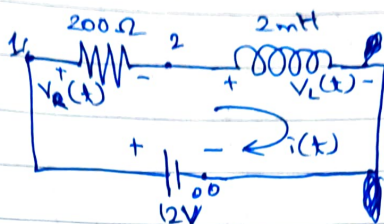Q-1- Plot $i(t)$, $V_R(t)$ and $V_L(t)$ for the given series RL circuit using PSPICE.



Q-2- Plot $i(t)$, $V_R(t)$ and $V_C(t)$ for the given series RC circuit using PSPICE.

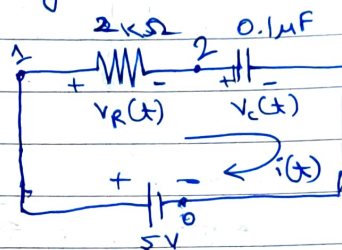ANSWERS:-

~~$$\textcircled{1} \quad Z = \frac{L}{R} = \frac{2 \text{ mH}}{200 \Omega} = 10^{-5} \text{ s}$$~~

~~$$\textcircled{1} \quad Z = \frac{L}{R} = \frac{2 \text{ mH}}{2 \text{ k}\Omega} = \frac{2 \times 10^{-3}}{2 \times 10^3} = 10^{-5} \text{ s}$$~~

~~$$\text{Display range} = 10Z = 10^{-4} \text{ s}$$~~

~~$$\text{Sampling gap} =$$~~

$$\textcircled{1} \quad Z = \frac{L}{R} = \frac{2 \text{ mH}}{2 \text{ k}\Omega} = 10^{-5} \text{ s} = \underline{\underline{10 \mu\text{s}}}$$

$$\text{Display range} = 10Z = \underline{\underline{100 \mu\text{s}}}$$

$$\text{Sampling gap} = \frac{10}{100} = \underline{\underline{1 \mu\text{s}}}$$

CODE :-

```

System LR circuit
V 1 0 DC DC 12
R 1 2 200
L 2 0 2m
.tran 1u 100u UI UIC
.probe
.end

```

_____X_____

(2) $T = R \times C = 2 \times 0.1 = \underline{\underline{0.2 \text{ ms}}}$

Display range = $10T = \underline{\underline{2 \text{ ms}}}$

Sampling gap = $\frac{T}{10} = \frac{0.2}{10} = \underline{\underline{0.02 \text{ ms}}}$ ~~0.2 ms~~

```


System RC circuit
V 1 0 DC 5
R 1 2 2K
C 2 0 0.1u
    0.02m
.tran 0.02m 2m UIC
.probe
.end

```

_____X_____

LAB

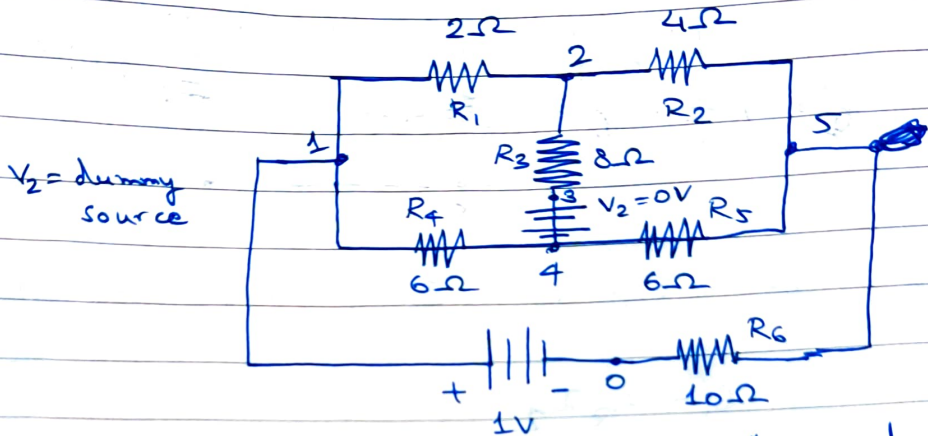4. Find out the current through the 8Ω resistor in the given circuit using PSpice and also verify reciprocity theorem.




DC analysis \rightarrow Operating point analysis

\rightarrow .op \odot
 \rightarrow view simulation output \square
 \rightarrow node voltages (listed)
 \rightarrow current through voltage sources


Ans DC Analysis

V1	1	0	DC	1
V2	3	4	DC	0
R1	1	2	2	
R2	2	5	4	
R3	2	3	8	
R4	1	4	6	
R5	4	5	6	
R6	5	0	10	

.op
 .end

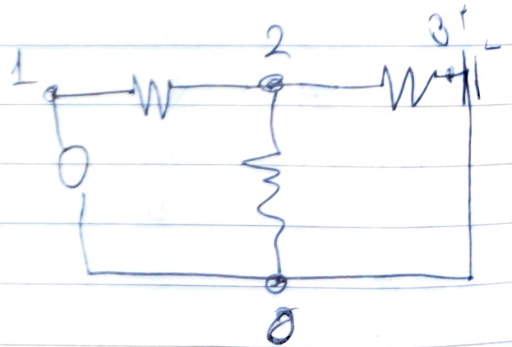

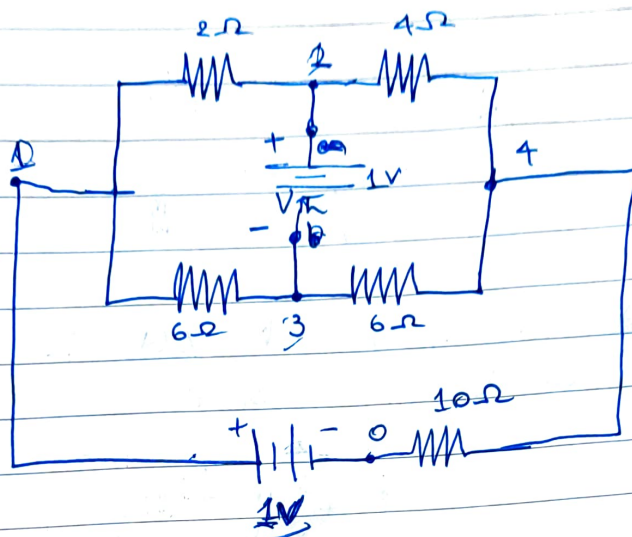- ⑤ Find out V_{Th} and R_{Th} for the given circuit between terminals A and B, using Pspice



$$\begin{aligned}
 V_{Th} &= V(2) - V(3) \\
 &= 0.9048 - 0.8571 \\
 &= 0.0477 \text{ V}
 \end{aligned}$$

$$R_{Th} = \frac{1\text{V (connected voltage)}}{I}$$

V	1	0	DC	1
R1	1	2	2	
R2	2	4	4	
R3	1	3	6	
R4	3	4	6	
R5	4	0	10	

.op
.end

$$= \frac{1}{2.266 \times 10^{-2}}$$

$$= 4.41 \Omega$$

$$\frac{0.0477}{1.079 \times 10^{-2}} = \frac{4.77}{1.079}$$

$$I_{sc} = 1.079 \times 10^{-2} \text{ A}$$

$$\Rightarrow I_N$$

V	1	2	DC	1
R1	0	1	2	
R2	1	3	4	
R3	0	2	6	
R4	2	3	6	
R5	3	0	10	

.op
.end


1/9/23

Lab.

using pspice

Q6:- Verify the compensation theorem for the following circuit, when value of the load R increases by 30%.

Ans:-

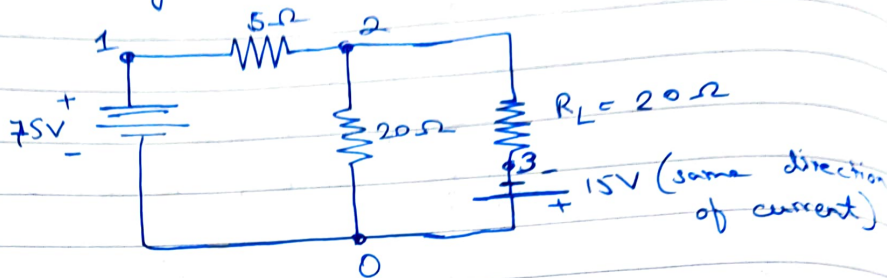

$$R_L = 20\Omega, I = 2.5A$$

$$R_L + \Delta R = 26\Omega, I_1 = 2A$$

$$\therefore V = I \times \Delta R$$

$$= 2.5 \times 6 = 15V$$

CODE:-1st case (dummy source)

Compensation

V1 1 0 DC 75

V2 0 3 DC 0

R1 1 2 5

R2 2 0 20

R3 2 3 20

.op
.end2nd case (30% output)


R3 2 3 26

.op
.end3rd case (voltage source added)


V2 3 0 DC -15

.op
.end

✓

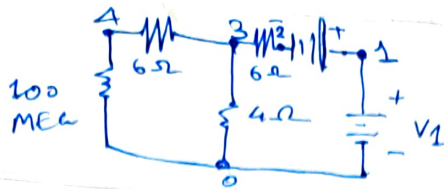

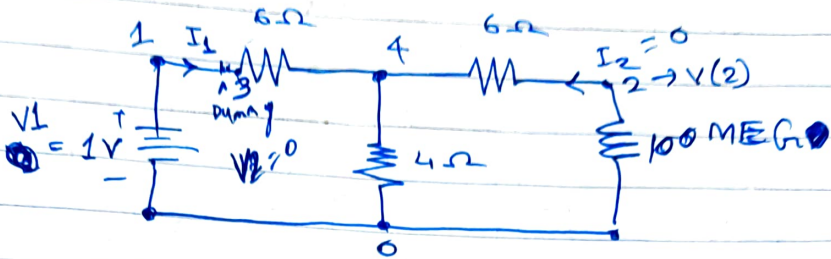7. Find out Z parameters for the given network using pspice.



Ans: $Z_{11} = 10\Omega$, $Z_{12} = 4\Omega$, $Z_{21} = 4\Omega$, $Z_{22} = 10\Omega$

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

Let $I_2 = 0$, $\therefore Z_{11} = \frac{V_1}{I_1}$, $Z_{21} = \frac{V_2}{I_1} \Rightarrow Z_{11} = 10, Z_{21} = 4$

Let $I_1 = 0$, $\therefore Z_{12} = \frac{V_1}{I_2}$, $Z_{22} = \frac{V_2}{I_2} \Rightarrow Z_{12} = 4, Z_{22} = 10$

for $I_2 = 0$,

```
V1 1 0 DC 1
V2 1 3 DC 0
R1 3 4 6
R2 4 2 6
R3 4 0 4
R4 2 0 100MEG
```

.op
end

for $I_1 = 0$,

```
V1 1 0 DC 1
V2 1 2 DC 0
R1 2 3 6
R2 3 4 6
R3 3 0 4
R4 4 0 100MEG
```

.op
end

14/9/23

TEST LAB


③ COMPENSATION THEOREM

classmate

Date

Page

- ③ Verify Compensation Theorem using PSpice for the following circuit when the value of load resistance decreases by 20%.

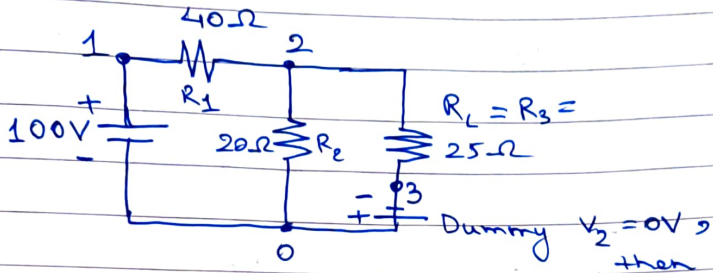Ans-

$$R_L = 25 \Omega$$

$$R_L \Delta R = 25 \Omega - \frac{20}{100} \times 25 \Omega = 20 \Omega$$

$$I(R_L) = \frac{100}{40 + 25} = 0.8696 \text{ A}$$

$$I_1(R_L - \Delta R) = 1 \text{ A}$$

$$\begin{aligned} \therefore \text{Voltage source needed} &= \Delta R \times I \\ &= 0.8696 \times 5 \text{ V} \\ &= 4.3480 \text{ V} \\ &= \underline{\underline{4.35 \text{ V (approx)}}} \end{aligned}$$

Voltage at V_2 was found to be 0.869 A again.

∴ Compensation Theorem verified

	Dummy source	Dummy source with R_L change	Compensation voltage source added
0.8696 x 5 4.3480	V1 1 0 DC 100 V2 3 0 DC 0 R1 1 2 40 R2 2 0 20 R3 2 3 25 .op .end	V1 1 0 DC 100 V2 3 0 DC 0 R1 1 2 40 R2 2 0 20 R3 2 3 20 .op .end	V1 1 0 DC 100 V2 3 0 DC 4.35 R1 1 2 40 R2 2 0 20 R3 2 3 20 .op .end