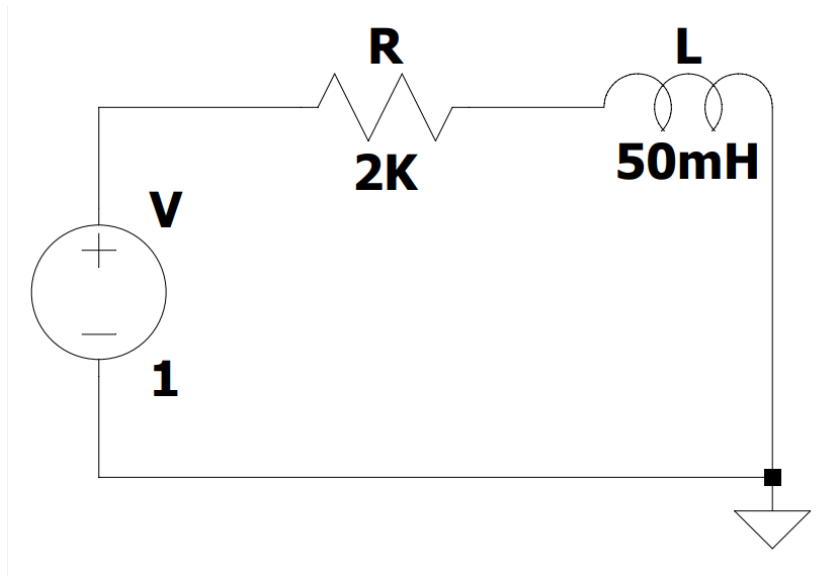


RL Circuit :

Plot $i(t)$, $V_R(t)$ and $V_L(t)$ for the given RL series circuit using Pspice.

**CODE:**

Series RL Circuit

```
V 1 0 DC 1
```

```
R 1 2 2K
```


```
L 2 0 50m
```

```
.TRAN 2.5u 250u UIC
```

```
.PROBE
```

```
.END
```


Output Plot:

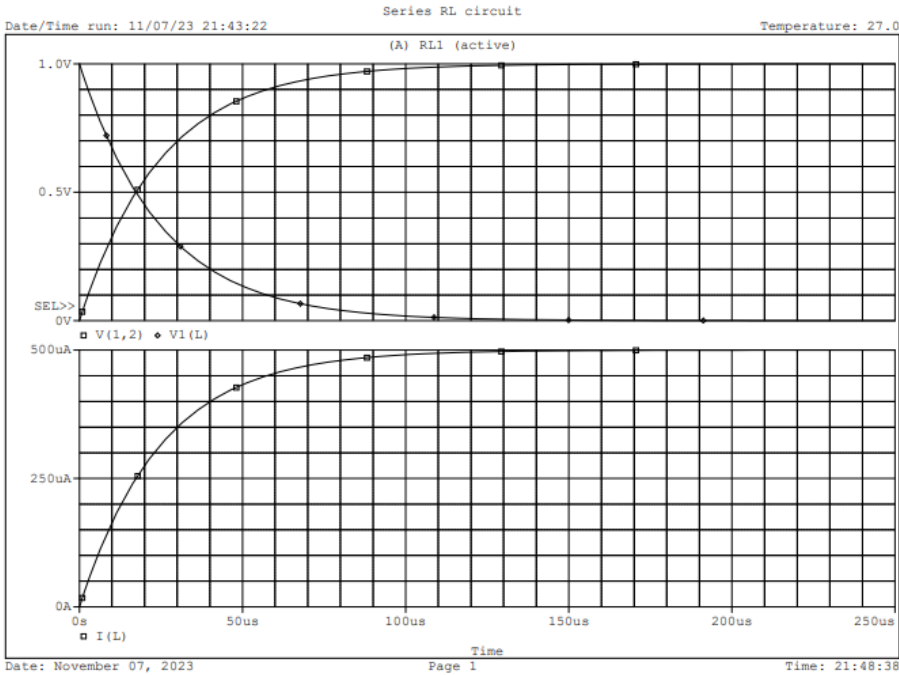

$V_R(t)$, $V_L(t)$ and $I_L(t)$ plots for series RC circuit

RC Circuit :

Plot $i(t)$, $V_R(t)$ and $V_C(t)$ for the given RL series circuit using Pspice.

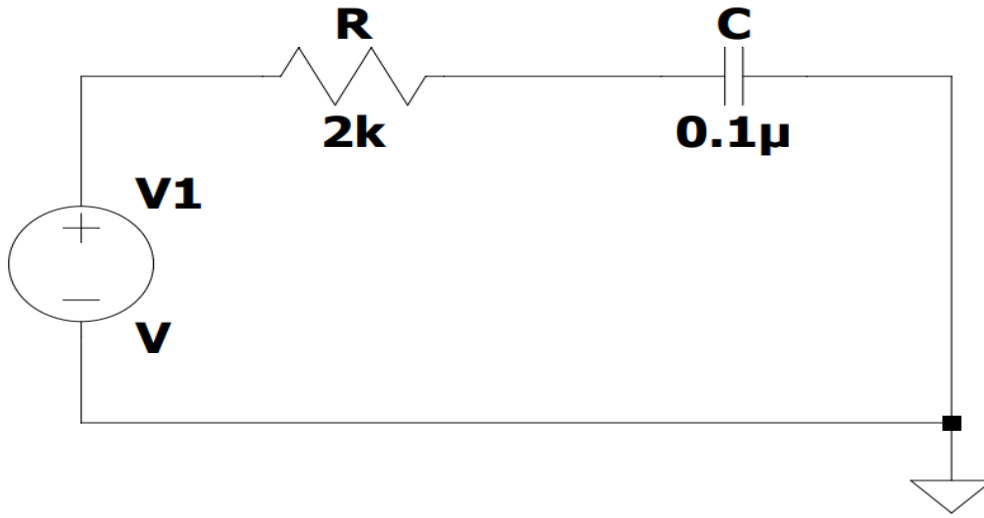**CODE:**

Series RC Circuit

V 1 0 DC 5

R 1 2 2K


C 2 0 0.1u

.TRAN 0.02m 2m UIC

.PROBE

.END


Output Plot:

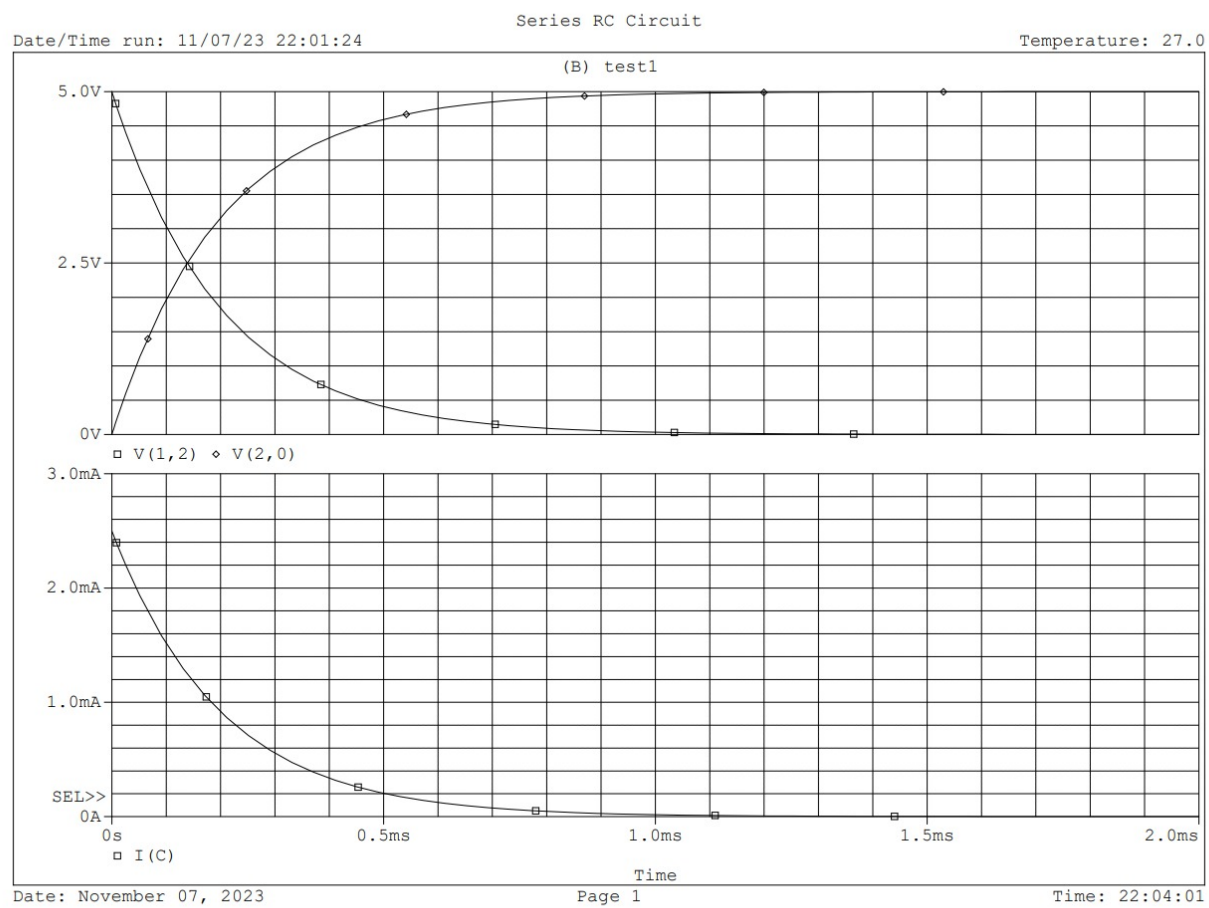

$V_R(t)$, $V_C(t)$ and $I_C(t)$ plots for series RC circuit

Thevenin Theorem:

Find out Thevenin Equivalent Circuit and find out V_{th} and R_{th} Using Pspice for the given circuit.

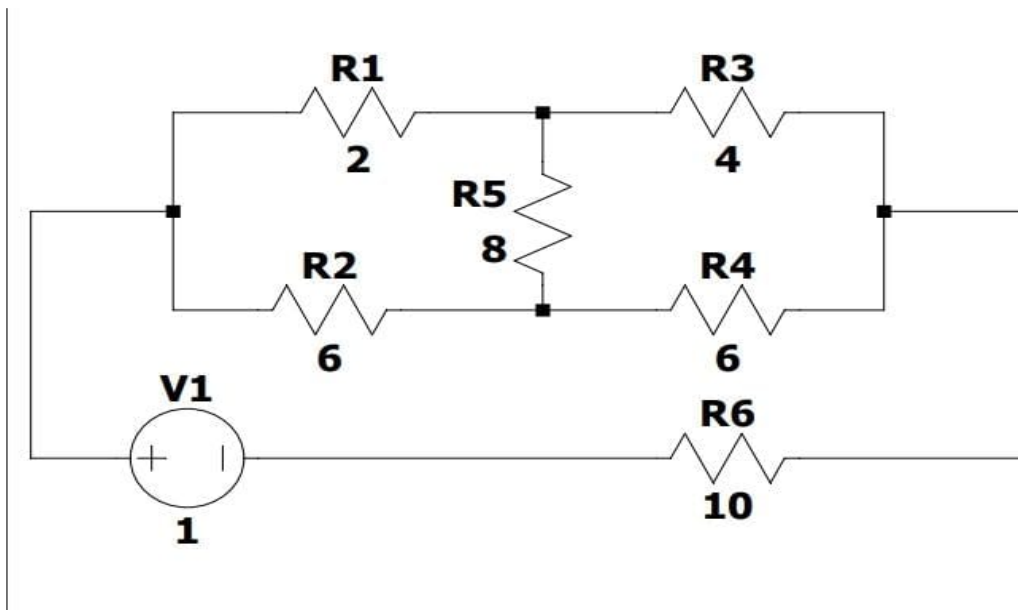

Case 1: Calculation of V_{th}

CODE

Calculation of V

V1 1 0 DC 1

R1 1 2 2

R2 2 4 4

R3 1 3 6

R4 3 4 6

R5 4 0 10

.OP

.END

OUTPUT

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
------	---------	------	---------	------	---------	------	---------


1	1.0000	2	.9048	3	.8571	4	.7143
---	--------	---	-------	---	-------	---	-------

VOLTAGE SOURCE CURRENTS

NAME	CURRENT
------	---------

V1	-7.143E-02
----	------------

$$V_{th} = V(2) - V(3) = 0.0477 \text{ V}$$

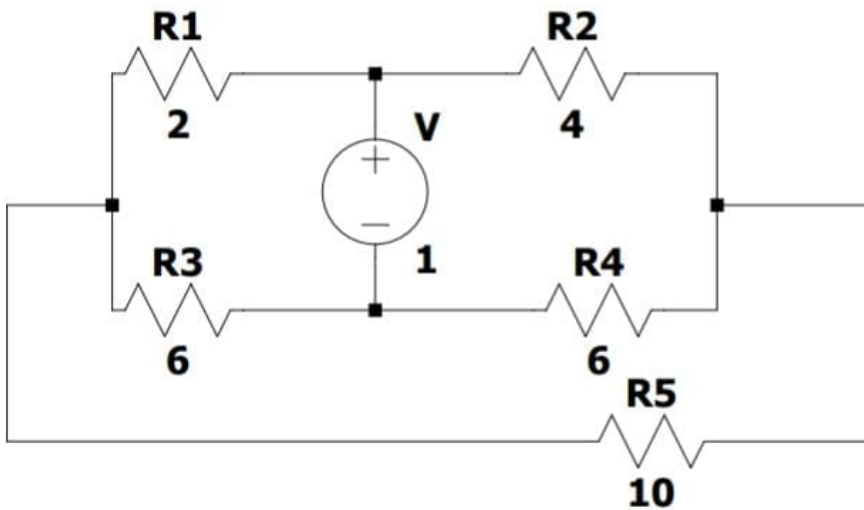Case 2: Calculation R_{th} **CODE**

Calculation of R

V 1 2 DC 1

R1 0 1 2

7

R2 1 3 4

R3 0 2 6

R4 2 3 6

R5 3 0 10

.OP

.END

OUTPUT

VOLTAGE SOURCE CURRENTS


NAME	CURRENT
V	2.266E 00

$R_{th} = 1 / 2.266 \text{ ohm}$

$= 4.41 \text{ ohm}$

Reciprocity Theorem:

Find out the current through the 8 ohm resistor in the given circuit using P-spice and verify reciprocity theorem.

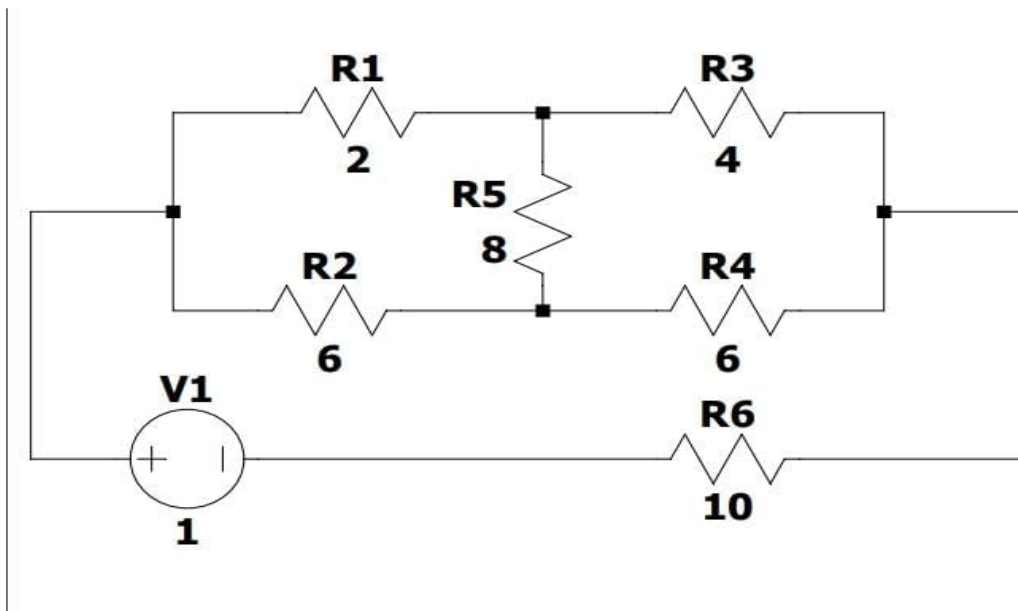**STEP-1**

Finding out the current through 8 ohm resistor

CODE:

DC Analysis

V1 0 1 DC 1

V2 4 3 DC 0

R1 1 2 2

R2 2 5 4

R3 2 3 8

R4 1 4 6

R5 4 5 6

R6 5 0 10


```
.op
.end
```

OUTPUT:

VOLTAGE SOURCE CURRENTS

NAME	CURRENT
V2	3.836E-03

STEP-2

Finding out the current through 8 ohm resistor

CODE:

DC Analysis

V2 0 1 DC 0

V1 4 3 DC 1

R1 1 2 2

R2 2 5 4

R3 2 3 8

R4 1 4 6

R5 4 5 6

R6 5 0 10

```
.op
```

```
.end
```

OUTPUT:

VOLTAGE SOURCE CURRENTS


NAME	CURRENT
V1	3.836E-03

Here, from the produced output we can notice that the current passing through V_2 , after swapping the sources, is equal to the current passing through V_1 . Hence, the Reciprocity theorem is proved and the value of current passing through 8 ohm resistor is 3.836 mA

Compensation Theorem:

Verify compensation theorem using PSpice for the given circuit when the value of R_L is increased by 30%.

Case 1: When R_3 is 20ohm.

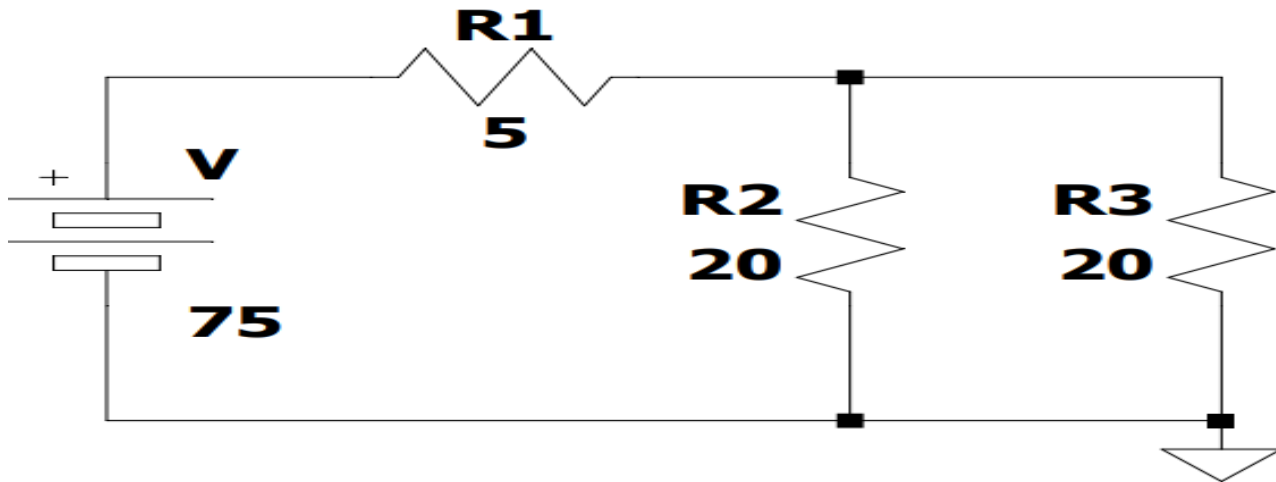

Case- 1: When R_3 is 20 ohm.

CODE

With given R value

```
V1 1 0 DC 75
```

```
V2 3 0 DC 0
```

```
R1 1 2 5
```

```
R2 2 0 20
```

```
R3 2 3 20
```

```
.OP
```


```
.END
```

OUTPUT

VOLTAGE SOURCE CURRENT

NAME	CURRENT
V1	-5.000E+00
V2	2.500E+00

Case- 2: When R3 is 26 ohm.

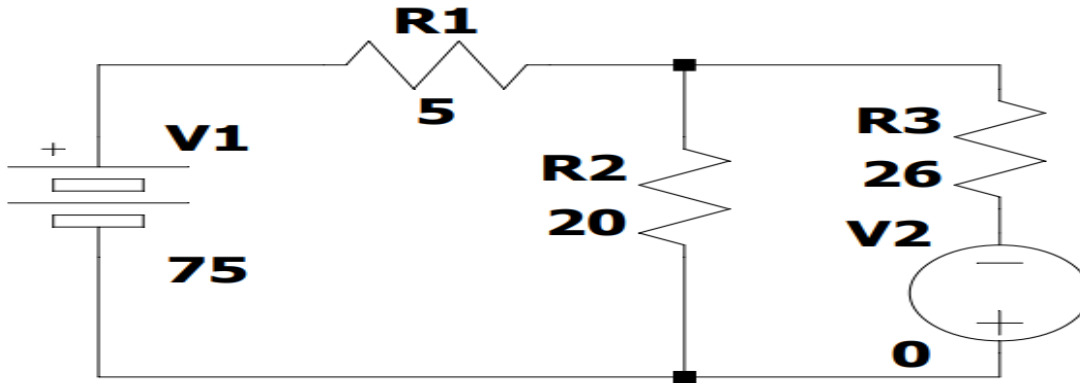

CODE

R value increased

V1 1 0 DC 75

V2 3 0 DC 0

R1 1 2 5

R2 2 0 20

R3 2 3 26

.OP

.END

OUTPUT


VOLTAGE SOURCE CURRENTS

NAME	CURRENT
------	---------

V1	-4.600E+00
----	------------

V2	2.000E+00
----	-----------

Case-3: When voltage source is added

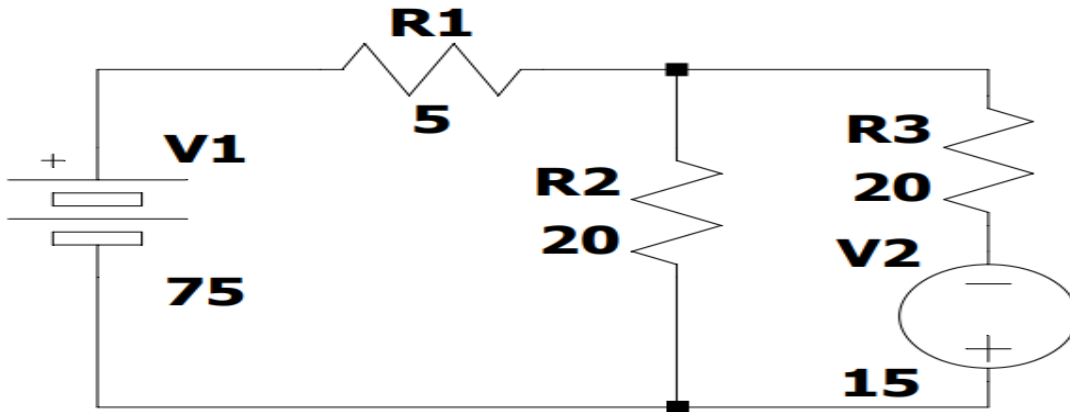

CODE

Compensated circuit

V1 1 0 DC 75

V2 3 0 DC -15

R1 1 2 5

R2 2 0 20

R3 2 3 26

.OP

.END


OUTPUT

VOLTAGE SOURCE CURRENTS

NAME	CURRENT
V1	-5.000E+00
V2	2.500E+00

Active Lowpass Filter:

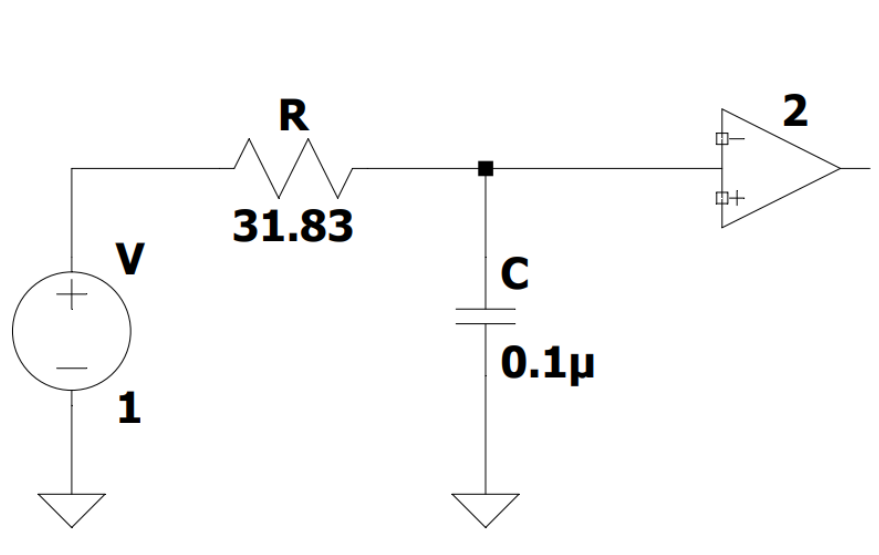Design a 1st order low-pass filter with cutoff frequency 50kHz and voltage gain 2. Plot the frequency response using P-Spice.



CODE:

Active LPF

V 1 0 AC 1

R 1 2 31.83

C 2 0 0.1u


E 3 0 2 0 2

.ac dec 1000 100Hz 1000kHz

.PROBE V_M(3,0) V_M(1,0)


.END

Output Plot:

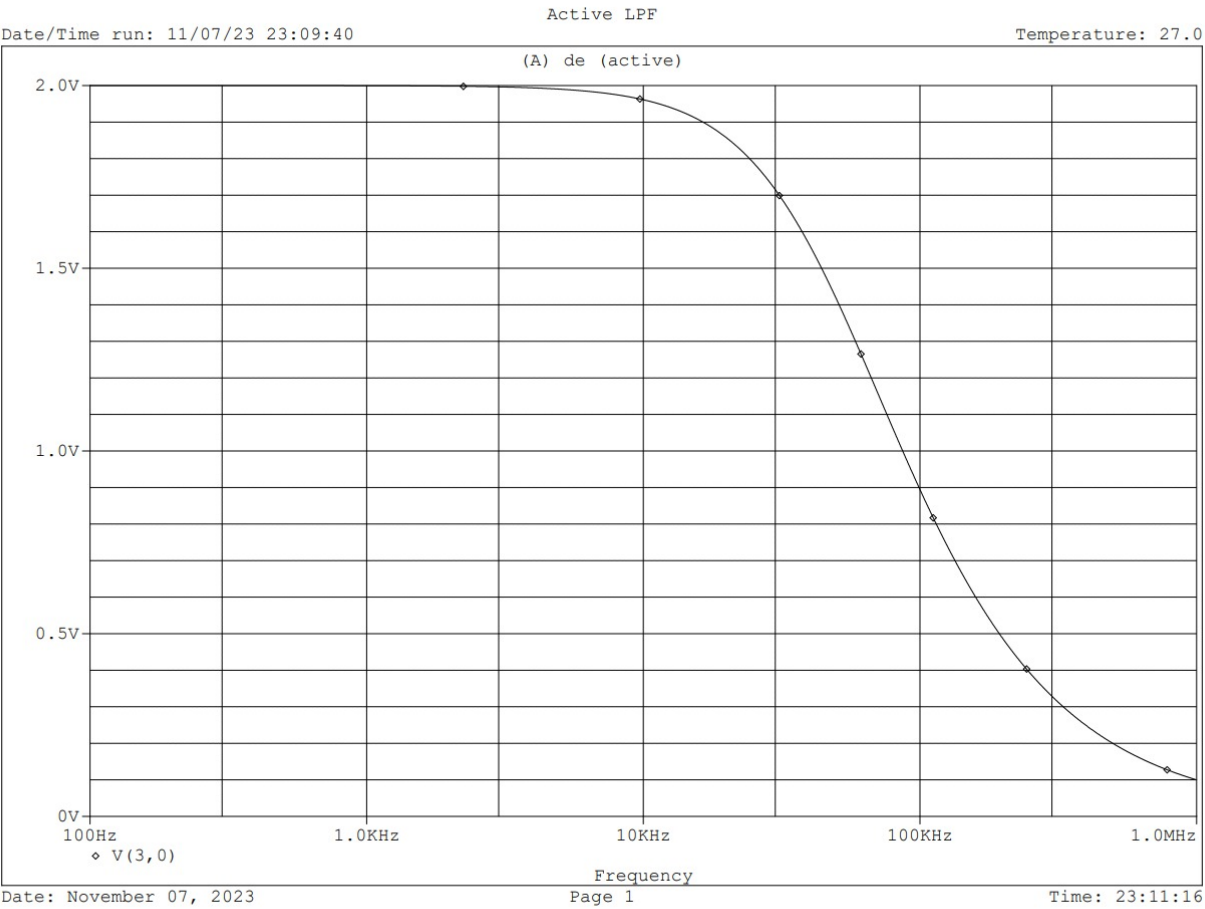

Active Highpass Filter:

Design a first order high pass filter with cutoff frequency 5KHz and voltage gain of 5. Plot the frequency response using Pspice.

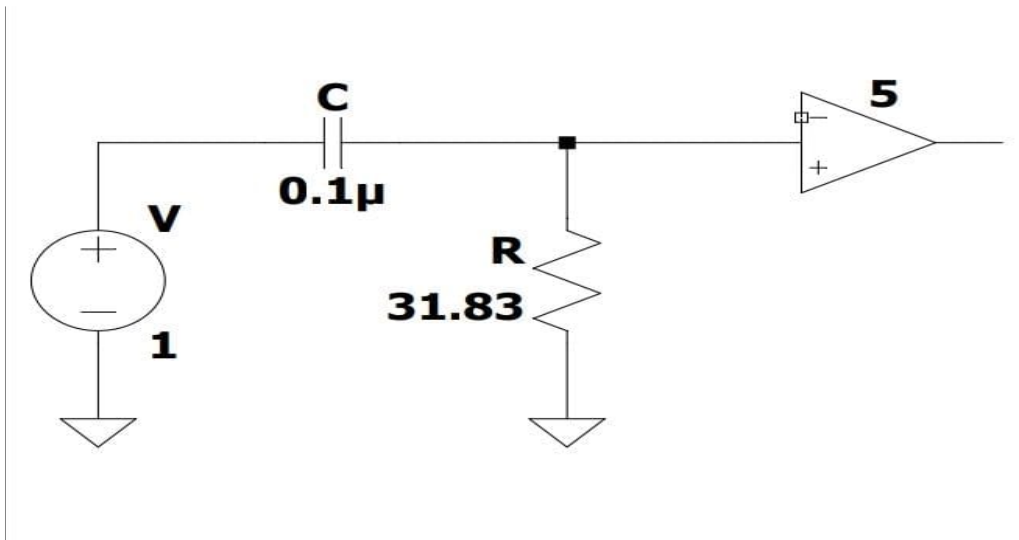**CODE:**

Active HPF

V 1 0 ac 1

C 1 2 0.1u

R 2 0 318.3


E 3 0 2 0 5

.ac dec 1000 100Hz 1000KHz


.PROBE V_M(3,0) V_M(1,0)

.END

Output Plot:

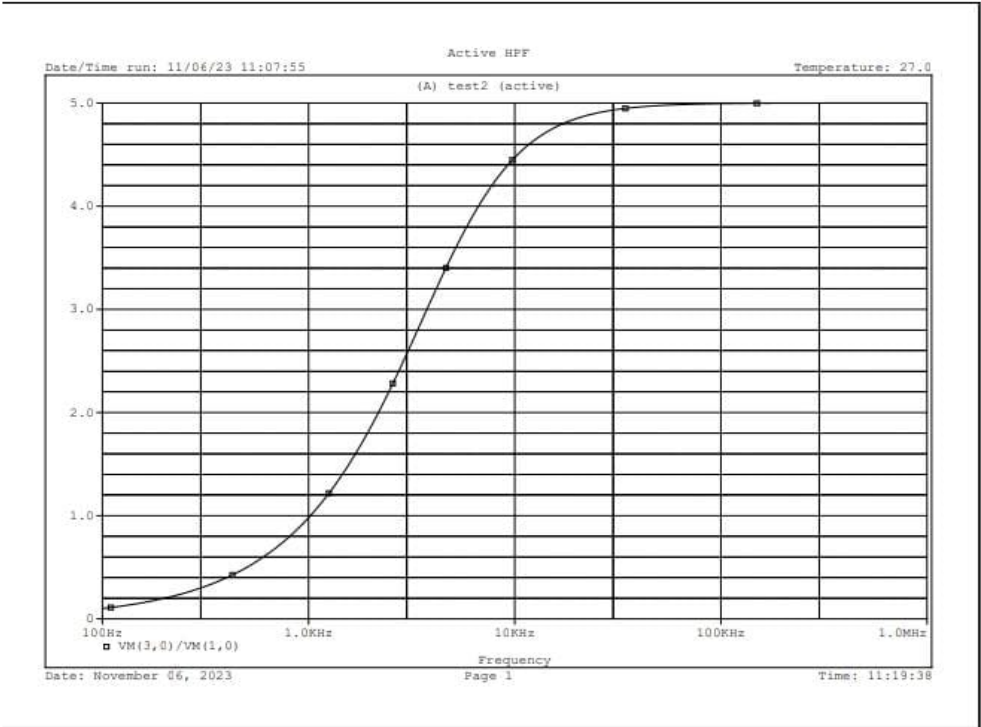

Active Bandpass Filter:

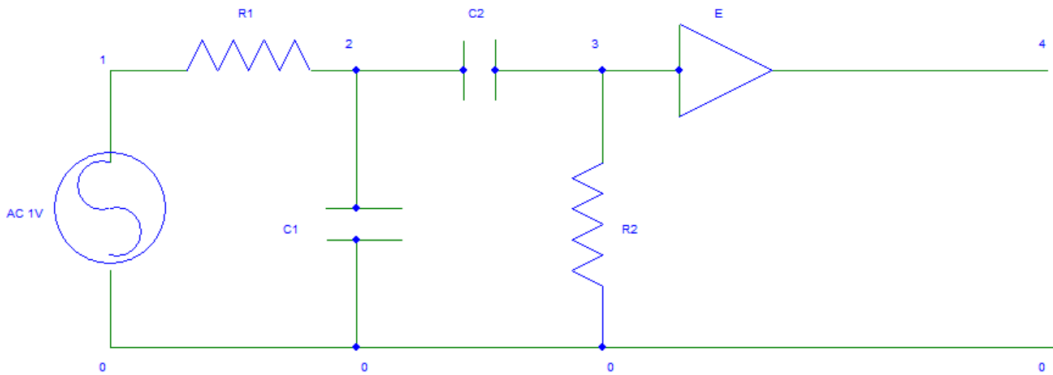

Band Pass Filter

V 1 0 AC 1

R1 1 2 318.3

C1 2 0 0.1u

C2 2 3 0.1u


R2 3 0 3.183

E 4 0 3 0 10

.ac dec 1000 5kHz 500kHz


.probe V_M(4,0) V_M(1,0)

.end

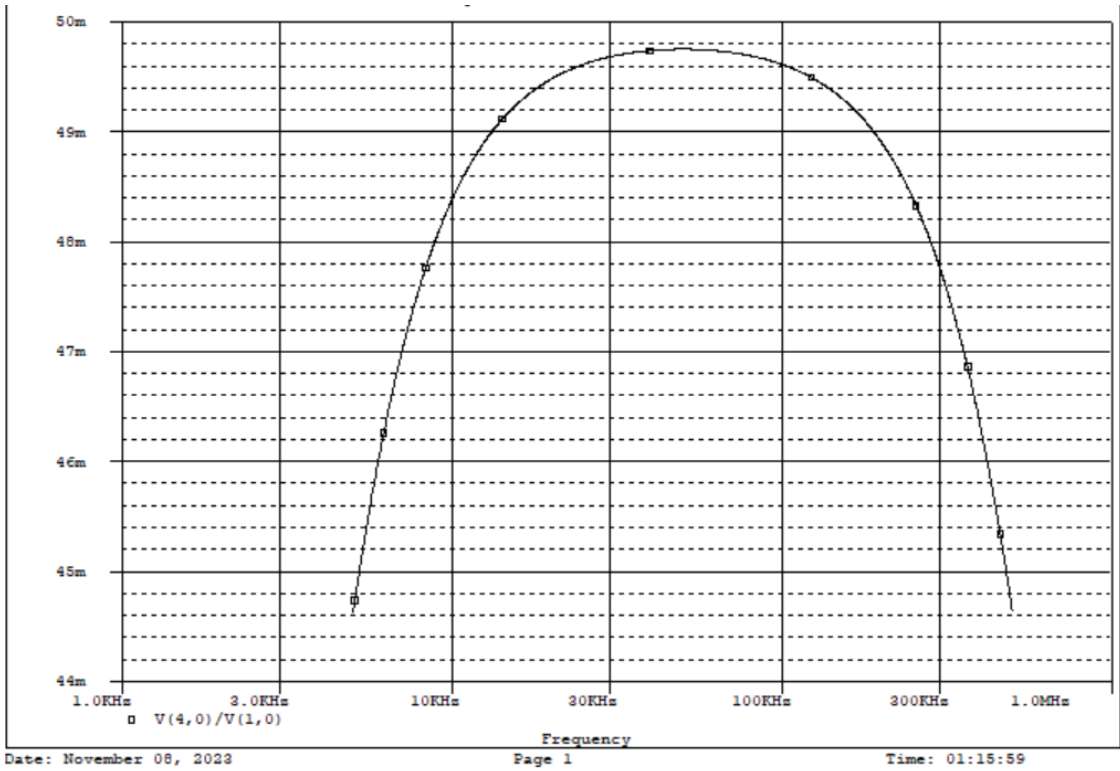


Y-parameter:

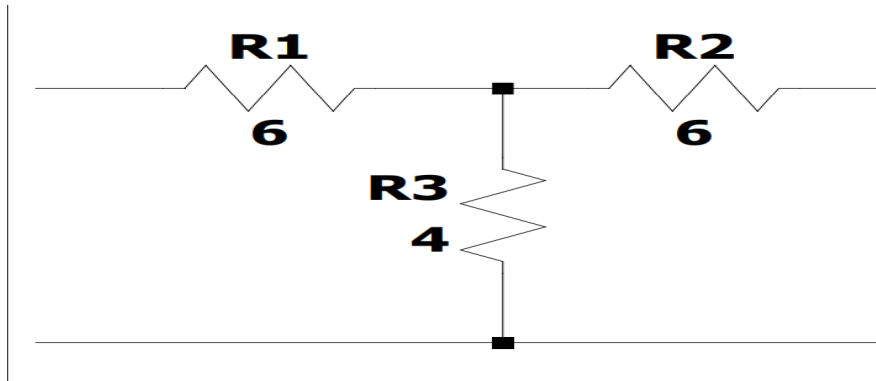Find out the Y-parameters for the given circuit using Pspice.



Case-1: When $V_1 = 0$.

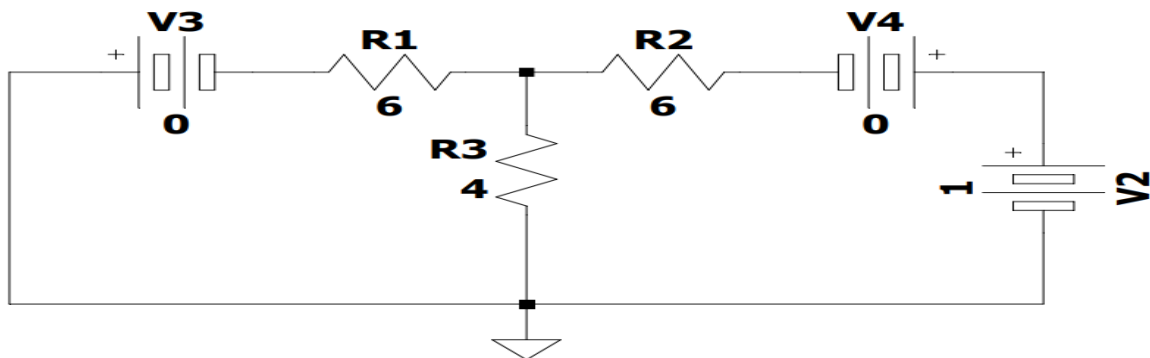

CODE:

V1 4 0 DC 1

V2 0 1 DC 0

V3 4 3 DC 0

R1 1 2 6

```

20
R2 2 3 6
R3 2 0 4
.OP
.END

```

OUTPUT:

Voltage source currents,


SOURCE	CURRENT
V2	-0.0476 A
V3	0.119 A

Now,

$$Y_{12} = \frac{I_1}{V_2} = \frac{-0.0476}{1} = -0.0476$$

$$Y_{22} = \frac{I_2}{V_2} = \frac{0.119}{1} = 0.119$$

Case-2: When $V_2 = 0$.

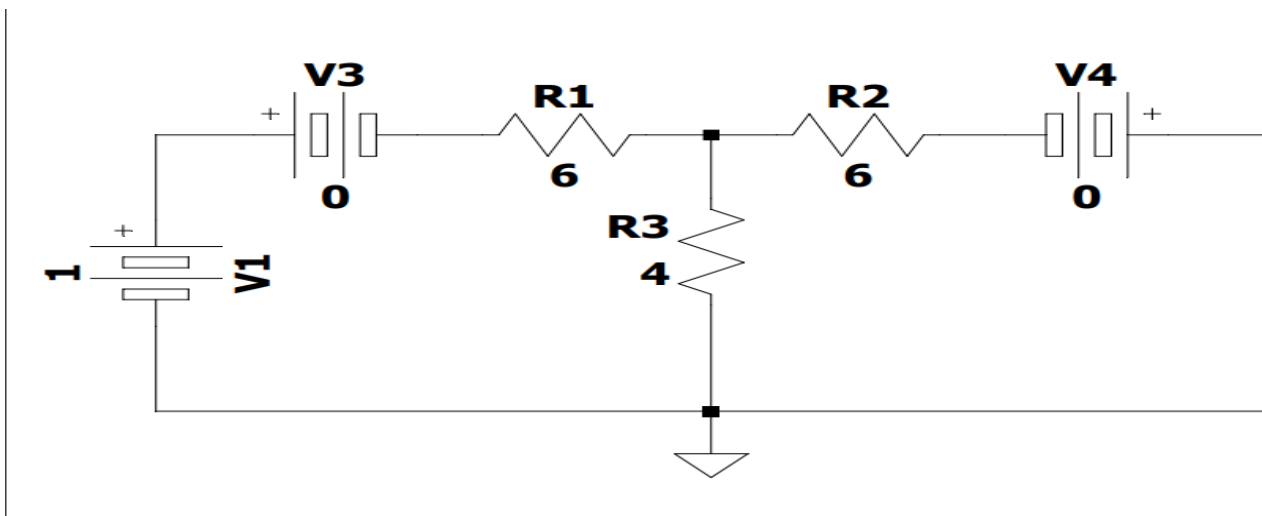

CODE:

```

V1 0 1 DC 1
V2 1 2 DC 0

```

21
V3 4 0 DC 0

R1 2 3 6

R2 3 4 6

R3 3 0 4

.OP

.END

OUTPUT:

Voltage source currents,

SOURCE	CURRENT
V2	0.119 A
V3	-0.0476 A


Now,

$$Y_{11} = \frac{I_1}{V_1} = \frac{0.119}{1} = 0.119$$


$$Y_{21} = \frac{I_2}{V_1} = \frac{-0.0476}{1} = -0.0476$$

Z-parameter:

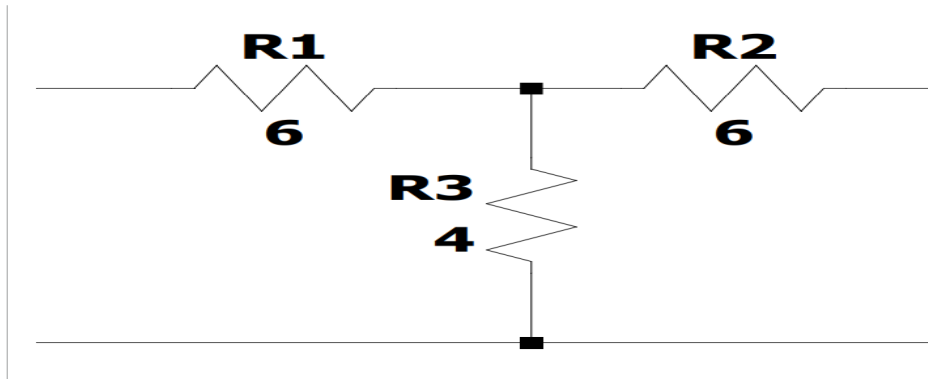Find out the Z-parameters for the given circuit using Pspice.



Case-1: When $I_1 = 0$

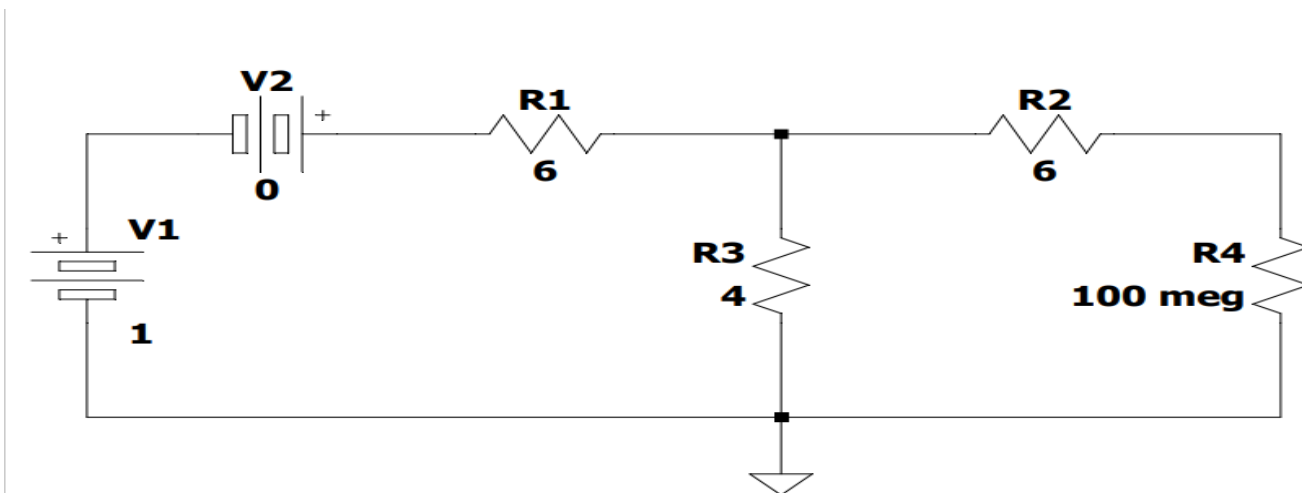**CODE:**

V1 1 0 DC 1

V3 1 2 DC 0

R1 2 3 6

R2 3 4 6

R3 3 0 4

R4 4 0 100meg

.OP

.END

OUTPUT:


Voltage source currents,

SOURCE	CURRENT
V1	0.25
V3	0.1

Now,

$$Z_{11} = 4 \text{ ohm}$$

$$Z_{12} = 10 \text{ ohm}$$

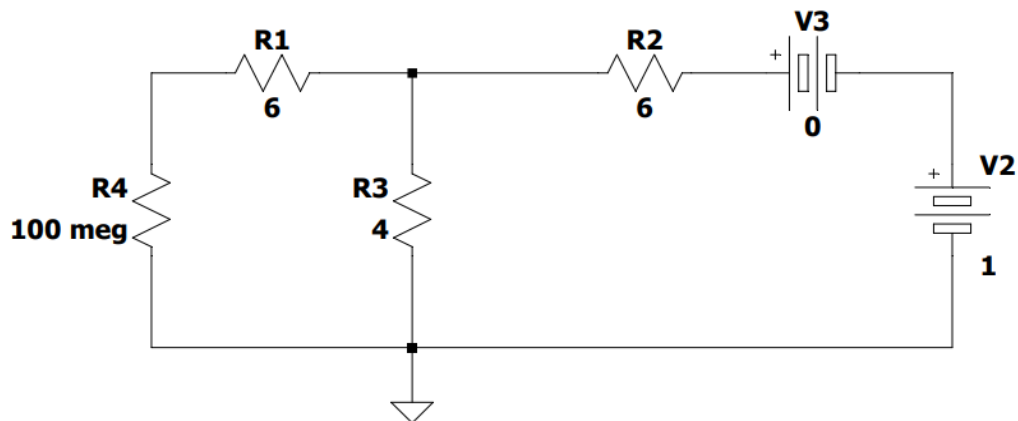Case-2: When $I_1 = 0$,**CODE:**

V1 1 0 DC 1

V3 1 2 DC 0

R1 1 2 6

R2 2 3 6

24

R3 2 0 4

R4 1 0 100meg

.OP

.END

OUTPUT:

Voltage source currents,

SOURCE	CURRENT
V2	0.25
V3	0.1

Now,

$$Z_{22} = 4 \text{ ohm}$$

$$Z_{21} = 10 \text{ ohm}$$